

mercury outboard starter solenoid wiring diagram

Mercury Outboard Starter Solenoid Wiring Diagram: A Detailed Guide for Boaters

mercury outboard starter solenoid wiring diagram is a crucial topic for anyone who owns or works on Mercury outboard motors. Whether you're troubleshooting a starting issue or planning to replace your starter solenoid, understanding the wiring diagram can save you time and frustration. In this article, we'll explore the ins and outs of the Mercury outboard starter solenoid wiring, discuss how the solenoid functions within the starting system, and provide practical tips for wiring and maintenance.

Understanding the Role of the Starter Solenoid in Mercury Outboards

When it comes to Mercury outboard engines, the starter solenoid acts as a high-current relay that controls the flow of electricity from the battery to the starter motor. Without the solenoid, the starter motor would not receive the necessary power to crank the engine. The solenoid also isolates the high current needed for starting from the ignition switch, protecting the switch and wiring from damage.

How the Starter Solenoid Works

The solenoid is essentially an electromagnet. When you turn the ignition key, a small electric current flows through the solenoid coil. This energizes the coil and creates a magnetic field that pulls a plunger or lever inside the solenoid. The movement of this plunger closes a set of heavy contacts, allowing high current from the battery to flow directly to the starter motor. Once the engine starts and you release the key, the current to the coil stops, and the solenoid disengages.

Breaking Down the Mercury Outboard Starter Solenoid Wiring Diagram

Having a clear wiring diagram is essential for diagnosing electrical problems or installing a new solenoid. While specific models and years may have slight variations, the core wiring principles remain consistent across Mercury outboards.

Key Components in the Wiring Diagram

A typical Mercury outboard starter solenoid wiring diagram includes the following elements:

- **Battery:** Supplies the electrical power.
- **Starter Solenoid:** The relay controlling the starter motor's power supply.
- **Starter Motor:** The motor that turns the engine over.
- **Ignition Switch:** Controls the activation of the solenoid coil.
- **Ground Connections:** Ensures proper circuit completion and safety.
- **Safety Switches (Neutral Safety or Kill Switch):** Prevents unintended starting or shutdowns.

Typical Wiring Connections

1. **Battery Positive Terminal to Solenoid Large Terminal:** The heavy gauge cable from the positive battery terminal connects to one of the large terminals on the solenoid. This is where the high current originates.
2. **Solenoid Large Terminal to Starter Motor:** The other large terminal on the solenoid connects directly to the starter motor's positive terminal.
3. **Ignition Switch to Solenoid Coil Terminal:** The ignition switch sends a low current signal to the solenoid coil terminal when turned to the "start" position.
4. **Solenoid Coil Ground:** The solenoid coil needs a ground connection, often connected to the engine block or battery negative terminal, to complete the circuit.
5. **Safety Switch Wiring:** Some Mercury outboards include safety switches that interrupt the solenoid coil circuit to prevent starting under unsafe conditions, such as when the engine is in gear.

Tips for Reading and Using Your Mercury Outboard Starter Solenoid Wiring Diagram

Understanding wiring diagrams can be intimidating at first, but with a few tips, you can make sense of the schematic and troubleshoot effectively.

Identify Symbols and Wire Colors

Most wiring diagrams use standard symbols for batteries, switches, solenoids, and motors. Familiarize

yourself with these symbols to follow the circuit more easily. Also, wire colors are often standardized: red for positive, black for ground, and other colors for control wires. Mercury wiring harnesses usually follow these conventions, but always refer to your specific model's manual.

Use a Multimeter for Testing

A multimeter is a boat owner's best friend when diagnosing starter solenoid issues. Use it to check for battery voltage at the solenoid terminals, verify continuity in the starter motor circuit, and test the ignition switch's output to the solenoid coil. This practical approach complements the wiring diagram and helps pinpoint faults.

Label Your Wires

If you need to disconnect wiring for repair or replacement, labeling wires before removal can prevent confusion during reassembly. This is especially important when working on older boats where the wiring may have been modified or damaged.

Common Mercury Outboard Starter Solenoid Wiring Issues

Understanding the wiring diagram can help you identify common problems that cause starting failures in Mercury outboards.

Corroded or Loose Connections

Exposure to moisture and saltwater can cause corrosion on battery terminals and solenoid connections. Loose or corroded terminals increase resistance, reducing current flow and preventing the

starter from engaging properly.

Faulty Ignition Switch or Safety Switch

If the ignition switch fails to send voltage to the solenoid coil, the starter won't activate. Similarly, a malfunctioning neutral safety switch can interrupt the coil circuit, blocking engine start.

Worn Solenoid Contacts

Inside the solenoid are heavy-duty contacts that open and close the starter circuit. Over time, these contacts can wear out or become pitted, preventing proper current flow even if the coil is energized.

Replacing or Upgrading Your Mercury Outboard Starter

Solenoid

If your starter solenoid is faulty, replacing it using the wiring diagram as a guide can restore reliable starting.

Choosing the Right Solenoid

Make sure the replacement solenoid matches your Mercury outboard's specifications, including voltage rating and terminal configuration. Many aftermarket solenoids are designed for universal applications but checking compatibility is crucial.

Step-by-Step Wiring Process

1. Disconnect the battery negative terminal to prevent shorts.
2. Remove the old solenoid and note all wire connections.
3. Connect the battery positive cable to the new solenoid's large terminal.
4. Attach the starter motor cable to the other large terminal.
5. Connect the ignition switch wire to the solenoid coil terminal.
6. Ensure the solenoid coil ground is properly connected.
7. Reconnect the battery and test the starting system.

Additional Resources and Tools for Mercury Outboard Electrical Work

For boat owners who want to deepen their knowledge, many resources provide detailed Mercury outboard wiring diagrams and electrical system overviews. Service manuals from Mercury Marine include comprehensive schematics tailored to specific engine models.

Online forums and boating communities are also excellent for sharing wiring tips and troubleshooting advice. Having the right tools, such as waterproof connectors, terminal cleaners, and a quality multimeter, will make electrical repairs smoother and more reliable.

Wiring the starter solenoid correctly is an essential step in maintaining the health of your Mercury outboard's starting system. The Mercury outboard starter solenoid wiring diagram serves as your roadmap to understanding how power flows from the battery to the starter motor and how control circuits work to safely engage the engine. With this knowledge, you're better equipped to diagnose issues, perform repairs, and keep your boat running smoothly on the water.

Frequently Asked Questions

What is a Mercury outboard starter solenoid wiring diagram used for?

A Mercury outboard starter solenoid wiring diagram is used to illustrate the electrical connections and wiring layout for the starter solenoid on Mercury outboard engines, helping in proper installation, troubleshooting, and repair.

Where can I find a reliable Mercury outboard starter solenoid wiring diagram?

Reliable Mercury outboard starter solenoid wiring diagrams can be found in the official Mercury Marine service manuals, on the Mercury Marine website, or through reputable boating forums and repair guides.

How do I identify the starter solenoid wires on a Mercury outboard motor?

Starter solenoid wires on a Mercury outboard motor typically include a battery positive wire, a wire from the ignition switch, and a wire to the starter motor. The wiring diagram will show the specific color codes and terminal locations.

What are the common wire colors used in Mercury outboard starter solenoid wiring?

Common wire colors include red for battery positive, black or brown for ground, and smaller gauge wires (often yellow or purple) for ignition or starter switch signals, although colors may vary by model and year.

Can I use a generic starter solenoid wiring diagram for my Mercury outboard motor?

While a generic wiring diagram might give a basic idea, it's important to use a model-specific Mercury outboard starter solenoid wiring diagram to ensure proper connections and avoid damage.

What should I check if my Mercury outboard starter solenoid is not working according to the wiring diagram?

Check for loose or corroded connections, ensure the battery is fully charged, verify the ignition switch wiring, and test the solenoid coil and contacts as indicated in the wiring diagram.

How do I wire a replacement starter solenoid on a Mercury outboard using the wiring diagram?

Using the wiring diagram, connect the battery positive cable to the solenoid's large terminal, connect the starter motor cable to the other large terminal, and attach the ignition switch wire to the small terminal. Ensure all connections are tight and corrosion-free.

Is it necessary to disconnect the battery before working on the Mercury outboard starter solenoid wiring?

Yes, it is important to disconnect the battery before working on the starter solenoid wiring to prevent electrical shock, short circuits, or accidental engine start.

How can I troubleshoot starter solenoid wiring issues using a Mercury outboard wiring diagram?

Use the wiring diagram to verify correct wire routing and connections, check continuity with a multimeter, inspect for damaged wires or corrosion, and test the solenoid coil and activation circuit to isolate the problem.

Additional Resources

Mercury Outboard Starter Solenoid Wiring Diagram: A Technical Exploration

mercury outboard starter solenoid wiring diagram serves as a crucial reference for marine technicians, boat owners, and DIY enthusiasts aiming to maintain or repair Mercury outboard engines.

Understanding the wiring configuration of the starter solenoid is essential, as it plays a pivotal role in the engine's starting mechanism. This article provides an in-depth examination of the wiring diagram, highlighting its practical applications, nuances, and implications for troubleshooting electrical issues in Mercury outboard motors.

Understanding the Role of the Starter Solenoid in Mercury Outboards

The starter solenoid in Mercury outboard engines functions as an electromagnetic switch that activates the starter motor, enabling the engine to crank. When the ignition key is turned to the start position, the solenoid receives a low-current signal, which closes a high-current circuit from the battery to the starter motor. This relay-like device is critical because it allows the heavy electrical load of the starter motor to be engaged without routing high current through the ignition switch, thereby preventing damage and ensuring longevity.

Key Components in the Wiring Diagram

A typical Mercury outboard starter solenoid wiring diagram includes several primary components interconnected to facilitate the starting process:

- **Battery:** Supplies electrical power to the starter circuit.
- **Ignition Switch:** Controls the solenoid's activation by sending a low-current start signal.
- **Starter Solenoid:** Acts as a relay that connects the battery to the starter motor.
- **Starter Motor:** Cranks the engine when energized.
- **Ground Connections:** Ensures proper circuit completion by connecting components to the negative battery terminal or engine block.

Each connection in the wiring diagram is meticulously designed to ensure reliable operation and safety. The solenoid is usually mounted near the starter motor to minimize voltage drop due to long wiring runs.

Decoding the Mercury Outboard Starter Solenoid Wiring Diagram

A comprehensive wiring diagram for a Mercury outboard starter solenoid typically illustrates how the solenoid terminals are connected to both the battery and ignition system. The diagram also clarifies wire gauge specifications, color codes, and terminal labels, which are essential for proper installation

and diagnosis.

Terminal Identification and Wire Color Coding

Mercury outboard solenoid terminals are generally marked as follows:

- **B+ or Battery Terminal:** Connects directly to the positive post of the battery.
- **S Terminal (Start):** Receives the small current from the ignition switch when starting.
- **M Terminal (Motor):** Connects to the starter motor's positive terminal.
- **Ground Terminal:** Provides a path to the negative battery terminal or engine ground.

Wiring color codes may vary slightly depending on the engine model year, but common colors include red for battery power, purple or yellow for the start signal, and black for ground. Consulting the exact wiring diagram for the specific Mercury outboard model is advised to avoid confusion.

Typical Wiring Sequence

Understanding the wiring flow is key to interpreting the Mercury outboard starter solenoid wiring diagram:

1. The positive battery cable connects to the solenoid's B+ terminal, supplying high current.

2. The ignition switch sends a low-current start signal to the S terminal on the solenoid.
3. When the S terminal is energized, the solenoid closes the internal contacts, allowing current to flow from B+ to the M terminal.
4. The M terminal feeds the starter motor, causing the engine to crank.
5. Ground connections complete the electrical circuit, ensuring proper function.

This sequence ensures the starter motor only draws full battery power during engine cranking, preventing damage to the ignition switch and wiring harness.

Practical Applications and Troubleshooting Insights

Having a clear Mercury outboard starter solenoid wiring diagram aids in diagnosing common electrical problems such as no-start conditions, intermittent starter engagement, or solenoid clicks without engine cranking.

Common Issues Identified Through Wiring Diagram Analysis

- **Faulty Solenoid Contacts:** If the solenoid fails to close the high-current circuit, the starter motor won't receive power despite receiving the start signal.
- **Corroded or Loose Battery Connections:** Voltage drop across corroded terminals can prevent the solenoid from energizing properly.

- **Damaged Ignition Switch Wiring:** A broken or shorted wire to the S terminal can inhibit the start signal.
- **Grounding Issues:** Poor ground connections can cause erratic solenoid behavior or failure.

By cross-referencing symptoms with the wiring diagram, technicians can systematically isolate and address electrical faults, improving repair efficiency.

Upgrading and Replacing Starter Solenoids

When replacing the starter solenoid or upgrading components, the wiring diagram ensures compatibility and correct installation. Some Mercury outboard models may use integrated solenoid-starter assemblies, while others have standalone solenoid units. Matching wire gauges and terminal configurations to the original specifications is vital to prevent electrical overload or insufficient current flow.

Comparative Overview: Mercury Outboard vs. Other Marine Starter Solenoids

While Mercury outboard starter solenoid wiring diagrams share fundamental principles with other marine engines, some distinctions exist:

- **Terminal Configuration:** Mercury often utilizes a simplified terminal setup compared to multi-terminal solenoids seen in certain Johnson or Evinrude engines.

- **Wire Gauge and Routing:** Mercury wiring harnesses tend to emphasize corrosion resistance and compact routing, reflecting the brand's design priorities.
- **Integration Level:** Mercury models may employ more integrated electronics, affecting solenoid wiring complexity.

These differences underscore the necessity of consulting model-specific wiring diagrams rather than relying on generic schematics.

Best Practices for Wiring and Maintenance

Maintaining the integrity of the starter solenoid wiring system involves:

- Regularly inspecting battery terminals and solenoid connections for corrosion.
- Ensuring all wires are securely fastened and free from abrasion.
- Using dielectric grease on terminals to prevent moisture intrusion.
- Verifying grounding points for tightness and cleanliness.
- Referencing the exact Mercury outboard starter solenoid wiring diagram during repairs.

Adhering to these practices extends the lifespan of electrical components and reduces the risk of starting failures.

Mercury outboard starter solenoid wiring diagrams reveal the intricate yet robust design behind one of the most critical systems in marine propulsion. Proper understanding and application of these diagrams facilitate effective maintenance and troubleshooting, enhancing both safety and performance on the water.

Mercury Outboard Starter Solenoid Wiring Diagram

mercury outboard starter solenoid wiring diagram: Outboard Engines Edwin R. Sherman, 1997 Outboard Engines fills the gap between owner's manuals that don't even tell you how to change a spark plug and professional shop manuals that detail how to do a complete rebuild. It covers basic principles and techniques for a wide variety of outboards - four-stroke as well as two-stroke - with the emphasis on maintenance and advanced troubleshooting. Ed Sherman's clear explanations and diagrams take you step by step through the basics and beyond, helping you track down even the most elusive problems a modern outboard can throw in your way. his methodical approach can save you a world of frustration - and peril - as well as time-and-a-half weekend mechanics' charges.

mercury outboard starter solenoid wiring diagram: Boating Magazine's Powerboater's Guide to Electrical Systems Edwin R. Sherman, 2000 Basic theory combined with a problem-solution format that provides step-by-step directions for repairs and add-ons.--Page 4 of cover.

mercury outboard starter solenoid wiring diagram: Seloc Mercury/Mariner Outboards, 1990-00 Repair Manual Scott A. Freeman, 1990

mercury outboard starter solenoid wiring diagram: Outboard Motor Service Manual Intertec Publishing, 1987 Detailed tips on periodic servicing, troubleshooting, general maintenance and repair are explicitly outlined in this manual. Repair is easy with the specifications and step-by-step repair procedures included for hundreds of models. Volume II covers models with 30hp and above.

mercury outboard starter solenoid wiring diagram: Outboard Motor Service Manual: Motors below 30 hp , 1979

mercury outboard starter solenoid wiring diagram: The Complete Book of Outboard Cruising Robert Scharff, 1960

mercury outboard starter solenoid wiring diagram: *Marine Engines and Equipment* Robert F. Latham, 1964

mercury outboard starter solenoid wiring diagram: The Complete Outboard Boating Manual Ernest A. Venk, 1958

mercury outboard starter solenoid wiring diagram: Electronic Servicing , 1957

mercury outboard starter solenoid wiring diagram: The Complete Book of Boating Ernest A. Zadig, 1976 Contains information on trailering, sailing, houseboating, outboards, motors, and electronics.

mercury outboard starter solenoid wiring diagram: Lakeland Boating , 1997

mercury outboard starter solenoid wiring diagram: British Automobiles Overseas , 1958

mercury outboard starter solenoid wiring diagram: *Popular Mechanics* , 1975-05 Popular Mechanics inspires, instructs and influences readers to help them master the modern world. Whether it's practical DIY home-improvement tips, gadgets and digital technology, information on the newest cars or the latest breakthroughs in science -- PM is the ultimate guide to our high-tech

lifestyle.

mercury outboard starter solenoid wiring diagram: Wiring Diagrams 1956-1989:
Outboard Motor and Inboard/Outdrive Penton Staff, 2000-05-24 A collection of wiring diagrams for vintage marine motors produced from 1956-1989.

Related to mercury outboard starter solenoid wiring diagram

Planet Compare - NASA Solar System Exploration NASA's real-time science encyclopedia of deep space exploration. Our scientists and far-ranging robots explore the wild frontiers of our solar system

Mercury 3D Model - NASA Solar System Exploration You are using an outdated browser. Please upgrade your browser to improve your experience

In Depth | Ganymede - NASA Solar System Exploration Not only is it the largest moon in our solar system, bigger than the planet Mercury and the dwarf planet Pluto, but NASA's Hubble Space Telescope has found the best evidence yet for an

In Depth | Our Solar System - NASA Solar System Exploration Our solar system consists of our star, the Sun, and everything bound to it by gravity - the planets Mercury, Venus, Earth, Mars, Jupiter, Saturn, Uranus, and Neptune; dwarf planets such as

RPS 3D Viewer - NASA Solar System Exploration Planets About Planets PLANETS Mercury Venus Earth Mars Jupiter Saturn Uranus Neptune DWARF PLANETS Pluto Ceres Makemake Haumea Eris HYPOTHETICAL

Mars By the Numbers - NASA Solar System Exploration Mars is the fourth planet from the Sun, and the seventh largest. It's the only planet we know of inhabited entirely by robots

In Depth | Titan - NASA Solar System Exploration Titan is bigger than Earth's moon, and larger than even the planet Mercury. This mammoth moon is the only moon in the solar system with a dense atmosphere, and it's the only world besides

In Depth | Callisto - NASA Solar System Exploration It's about the same size as Mercury. In the past, some scientists thought of Callisto as a boring "ugly duckling moon" and a "hunk of rock and ice." That's because the crater-covered world

In Depth | Moons - NASA Solar System Exploration Of the terrestrial (rocky) planets of the inner solar system, neither Mercury nor Venus have any moons at all, Earth has one and Mars has its two small moons. In the outer solar system, the

In Depth | Earth's Moon - NASA Solar System Exploration The brightest and largest object in our night sky, the Moon makes Earth a more livable planet by moderating our home planet's wobble on its axis, leading to a relatively stable climate. It also

Planet Compare - NASA Solar System Exploration NASA's real-time science encyclopedia of deep space exploration. Our scientists and far-ranging robots explore the wild frontiers of our solar system

Mercury 3D Model - NASA Solar System Exploration You are using an outdated browser. Please upgrade your browser to improve your experience

In Depth | Ganymede - NASA Solar System Exploration Not only is it the largest moon in our solar system, bigger than the planet Mercury and the dwarf planet Pluto, but NASA's Hubble Space Telescope has found the best evidence yet for an

In Depth | Our Solar System - NASA Solar System Exploration Our solar system consists of our star, the Sun, and everything bound to it by gravity - the planets Mercury, Venus, Earth, Mars, Jupiter, Saturn, Uranus, and Neptune; dwarf planets such as

RPS 3D Viewer - NASA Solar System Exploration Planets About Planets PLANETS Mercury Venus Earth Mars Jupiter Saturn Uranus Neptune DWARF PLANETS Pluto Ceres Makemake Haumea Eris HYPOTHETICAL

Mars By the Numbers - NASA Solar System Exploration Mars is the fourth planet from the Sun, and the seventh largest. It's the only planet we know of inhabited entirely by robots

In Depth | Titan - NASA Solar System Exploration Titan is bigger than Earth's moon, and larger than even the planet Mercury. This mammoth moon is the only moon in the solar system with a dense atmosphere, and it's the only world besides

In Depth | Callisto - NASA Solar System Exploration It's about the same size as Mercury. In the past, some scientists thought of Callisto as a boring "ugly duckling moon" and a "hunk of rock and ice." That's because the crater-covered world

In Depth | Moons - NASA Solar System Exploration Of the terrestrial (rocky) planets of the inner solar system, neither Mercury nor Venus have any moons at all, Earth has one and Mars has its two small moons. In the outer solar system, the

In Depth | Earth's Moon - NASA Solar System Exploration The brightest and largest object in our night sky, the Moon makes Earth a more livable planet by moderating our home planet's wobble on its axis, leading to a relatively stable climate. It also

Planet Compare - NASA Solar System Exploration NASA's real-time science encyclopedia of deep space exploration. Our scientists and far-ranging robots explore the wild frontiers of our solar system

Mercury 3D Model - NASA Solar System Exploration You are using an outdated browser. Please upgrade your browser to improve your experience

In Depth | Ganymede - NASA Solar System Exploration Not only is it the largest moon in our solar system, bigger than the planet Mercury and the dwarf planet Pluto, but NASA's Hubble Space Telescope has found the best evidence yet for an

In Depth | Our Solar System - NASA Solar System Exploration Our solar system consists of our star, the Sun, and everything bound to it by gravity - the planets Mercury, Venus, Earth, Mars, Jupiter, Saturn, Uranus, and Neptune; dwarf planets such as

RPS 3D Viewer - NASA Solar System Exploration Planets About Planets PLANETS Mercury Venus Earth Mars Jupiter Saturn Uranus Neptune DWARF PLANETS Pluto Ceres Makemake Haumea Eris HYPOTHETICAL

Mars By the Numbers - NASA Solar System Exploration Mars is the fourth planet from the Sun, and the seventh largest. It's the only planet we know of inhabited entirely by robots

In Depth | Titan - NASA Solar System Exploration Titan is bigger than Earth's moon, and larger than even the planet Mercury. This mammoth moon is the only moon in the solar system with a dense atmosphere, and it's the only world besides

In Depth | Callisto - NASA Solar System Exploration It's about the same size as Mercury. In the past, some scientists thought of Callisto as a boring "ugly duckling moon" and a "hunk of rock and ice." That's because the crater-covered world

In Depth | Moons - NASA Solar System Exploration Of the terrestrial (rocky) planets of the inner solar system, neither Mercury nor Venus have any moons at all, Earth has one and Mars has its two small moons. In the outer solar system, the

In Depth | Earth's Moon - NASA Solar System Exploration The brightest and largest object in our night sky, the Moon makes Earth a more livable planet by moderating our home planet's wobble on its axis, leading to a relatively stable climate. It also

Planet Compare - NASA Solar System Exploration NASA's real-time science encyclopedia of deep space exploration. Our scientists and far-ranging robots explore the wild frontiers of our solar system

Mercury 3D Model - NASA Solar System Exploration You are using an outdated browser. Please upgrade your browser to improve your experience

In Depth | Ganymede - NASA Solar System Exploration Not only is it the largest moon in our solar system, bigger than the planet Mercury and the dwarf planet Pluto, but NASA's Hubble Space Telescope has found the best evidence yet for an

In Depth | Our Solar System - NASA Solar System Exploration Our solar system consists of our star, the Sun, and everything bound to it by gravity - the planets Mercury, Venus, Earth, Mars, Jupiter, Saturn, Uranus, and Neptune; dwarf planets such as

RPS 3D Viewer - NASA Solar System Exploration Planets About Planets PLANETS Mercury Venus Earth Mars Jupiter Saturn Uranus Neptune DWARF PLANETS Pluto Ceres Makemake Haumea Eris HYPOTHETICAL

Mars By the Numbers - NASA Solar System Exploration Mars is the fourth planet from the Sun, and the seventh largest. It's the only planet we know of inhabited entirely by robots

In Depth | Titan - NASA Solar System Exploration Titan is bigger than Earth's moon, and larger than even the planet Mercury. This mammoth moon is the only moon in the solar system with a dense atmosphere, and it's the only world besides

In Depth | Callisto - NASA Solar System Exploration It's about the same size as Mercury. In the past, some scientists thought of Callisto as a boring "ugly duckling moon" and a "hunk of rock and ice." That's because the crater-covered world

In Depth | Moons - NASA Solar System Exploration Of the terrestrial (rocky) planets of the inner solar system, neither Mercury nor Venus have any moons at all, Earth has one and Mars has its two small moons. In the outer solar system, the

In Depth | Earth's Moon - NASA Solar System Exploration The brightest and largest object in our night sky, the Moon makes Earth a more livable planet by moderating our home planet's wobble on its axis, leading to a relatively stable climate. It also

Related Articles

- [arcs and central angles worksheet](#)
- [california united states history the twentieth century](#)
- [are you afraid of the dark](#)

[Back to Home](#)